

Total No. of Questions :8]

SEAT No. :

P4027

[5351]-107

[Total No. of Pages : 2

F.E.

BASIC ELECTRONICS ENGINEERING
(2015 Pattern) (Semester - I & II)

Time : 2 Hours]

[Max. Marks : 50

Instructions to the candidates:

- 1) Figures to the right indicate full marks.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Assume suitable data, if necessary.

Q1) a) Define rectifier circuit and mention its types. Draw and explain any one with waveforms. [6]


b) Draw a circuit diagram of CE amplifier. State the function of each component in the circuit. [6]

OR

Q2) a) Explain construction of Enhancement type N-channel MOSFET. [6]

b) Draw and explain Voltage Multiplier circuit. [6]

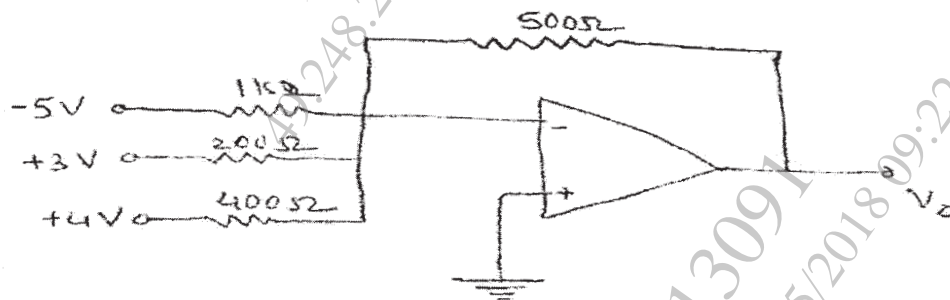Q3) a) Find output voltage of op-amp circuit shown in fig. below, [6]



b) Draw 2 input Ex-OR gate, write logic equation and implement using basic logic gates. [6]

OR

Q4) a) Draw and explain circuit diagram of Astable Multivibrator using IC 555. Write equation for frequency of oscillations. [6]

b) Draw block diagram of Microprocessor and Microcontroller. [6]

P.T.O.

Q5) a) Draw and explain block diagram of Digital Thermometer. Mention two applications. [7]

b) Compare active and passive transducers. [6]

OR

Q6) a) Explain in detail : [7]

i) Construction of DIAC.

ii) Characteristics of DIAC.

iii) Modes of operation

b) Explain in detail, the selection criteria for transducer. [6]

Q7) a) Explain the elements of communication system with the help of block diagram. [7]

b) Write a note on co-axial cable and optical fiber cable with neat structural diagram. [6]

OR

Q8) a) Explain the basic structure of mobile phone system. [6]

b) A carrier signal $20\sin(2\pi \times 104t)$ is used to modulating signal $10 \sin (2\pi \times 103t)$. Determine the modulation index for the modulated wave and draw the frequency spectrum for AM wave. [7]

